

# Computer Organization and Architecture, Pt. 1

*Charles Abzug, Ph.D.*

Department of Computer Science  
James Madison University  
Harrisonburg, VA 22807

Voice Phone: 540-568-8746, E-mail:  
CharlesAbzug@ACM.org

Home Page: <http://www.cs.jmu.edu/users/abzugcx>

# **Carpinelli Table 1.1: BASIC BOOLEAN FUNCTIONS I**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Table 1.2: BASIC BOOLEAN FUNCTIONS II**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Notation for Boolean Logical Operations

$$A' \equiv \bar{A} \equiv \sim A \equiv !A \equiv \text{NOT } A$$

$$X \vee Y \equiv X + Y \equiv \text{X OR Y}$$

$$X \wedge Y \equiv X \cdot Y \equiv XY \equiv \text{X AND Y}$$

X NAND Y

X NOR Y

$$X \oplus Y \equiv \text{X XOR Y}$$

X XNOR Y

# Carpinelli Table 1.3: ALL POSSIBLE BOOLEAN FUNCTIONS of TWO INPUT VARIABLES

$x \wedge y$					$x \oplus y$					$x \vee y$								
↓					↓					↓								
$x$	$y$	$0$	$\wedge$	$xy'$	$x$	$x'y$	$y$	$\oplus$	$\vee$	NOR	XNOR	$y'$	$x + y'$	$x'$	$x' + y$	NAND	$1$	
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Table 1.4:  
TRUTH TABLE for a  
COMPOSITE BOOLEAN FUNCTION**

$$F(x,y) = x \cdot y' + y \cdot z$$

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Table 1.5:  
TRUTH TABLE for another  
COMPOSITE BOOLEAN FUNCTION**

$$F(x,y) = (x + y') \cdot (y + z)$$

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Table 1.6:  
TRUTH TABLES DEMONSTRATING  
ALGEBRAIC EQUIVALENCES RESULTING from  
DeMORGAN'S THEOREMS**

$$F(x,y) = (x \bullet y' + y \bullet z)' = (x' + y) \bullet (y' + z) = x' \bullet y' + x' \bullet z' + y \bullet z'$$

Original figure or table © 2001 by Addison Wesley Longman, Inc



# **Carpinelli Figure 1.1: BASIC KARNAUGH MAPS (3-variable and 4-variable)**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Figure 1.2: GENERATION of GRAY CODE**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 1.3:  
SAMPLE 3-VARIABLE KARNAUGH MAP  
SHOWING ALGEBRAIC SIMPLIFICATION**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 1.4:  
SAMPLE 4-VARIABLE KARNAUGH MAP  
SHOWING ALGEBRAIC SIMPLIFICATION**

Original figure or table © 2001 by Addison Wesley Longman, Inc


**Carpinelli Figure 1.5 :**  
**ANOTHER 4-VARIABLE KARNAUGH MAP**  
**SHOWING ALGEBRAIC SIMPLIFICATION**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.7: LOGIC CIRCUITS IMPLEMENTING a BOOLEAN FUNCTION

Original figure or table © 2001 by Addison Wesley Longman, Inc

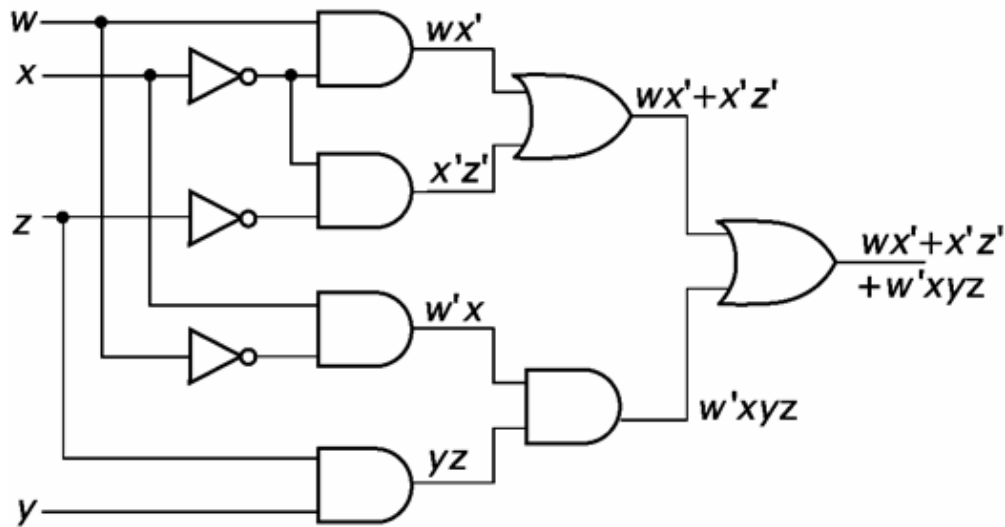
# Carpinelli Figure 1.7: LOGIC CIRCUITS IMPLEMENTING a BOOLEAN FUNCTION



(a)

**NOTE:** This is a three-stage circuit — first stage AND gates, second stage one OR and one AND gate, third stage an OR gate. This is not how we implement a Boolean function normally.

 Original figure or table © 2001 by Addison Wesley Longman, Inc



(b)

This is a normal logic-circuit implementation of a Boolean function.

# **Carpinelli Figure 1.8: SIMPLE BUFFER GATE and TRI-STATE GATES**

Original figure or table © 2001 by Addison Wesley Longman, Inc



# Carpinelli Table 1.7, as it appears in the text: TRUTH TABLES for BUFFER GATES

**Simple Buffer  
Gate**

**Tri-State Buffer  
(Active-High Enable)**

**Tri-State Buffer  
(Active-Low Enable)**

Original figure or table © 2001 by Addison Wesley Longman, Inc


# Carpinelli Table 1.7, TRUTH TABLES FOR BUFFER GATES *CORRECTED* to COUNTING ORDER:

Simple Buffer Gate

INPUT	OUTPUT
0	0
1	1


Tri-State Buffer  
(Active-High Enable)

INPUT	E	OUTPUT
X	1	Z
0	0	0
1	1	1

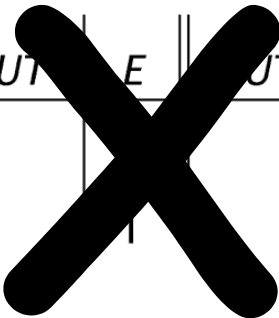

Tri-State Buffer  
(Active-Low Enable)

INPUT	E	OUTPUT
0	0	0
1	1	1
X	0	Z

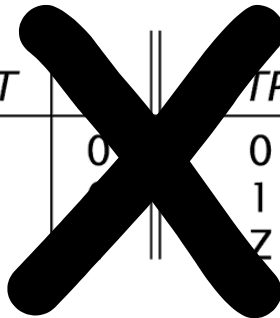


Original figure or table © 2001 by Addison Wesley Longman, Inc

Truth Tables in  
Counting Order:

<i>E</i>	<i>In</i>	<i>Out</i>
0	X	Z
1	0	0
1	1	1

<i>E</i>	<i>In</i>	<i>Out</i>
0	0	0
0	1	1
1	X	Z
 
# BCD-to-Seven-Segment Decoder: SEGMENT LABELS



# Carpinelli Figure 1.22: BCD-to-SEVEN-SEGMENT DECODERS: TRUTH TABLES for all SEVEN BOOLEAN FUNCTIONS

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.23 (a): KARNAUGH MAP SIMPLIFICATION of TWO BOOLEAN FUNCTIONS

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 1.23 (b):  
LOGICAL CIRCUITS IMPLEMENTING  
TWO BOOLEAN FUNCTIONS**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.9 (a): MULTIPLEXOR


Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.9 (b), as it appears in the text:

Original figure or table © 2001 by Addison Wesley Longman, Inc


 
# Carpinelli Figure 1.9 (b), *CORRECTED*:



$S_1$	$S_0$	$E$	Output
X	X	0	Z
0	0	1	Input 0
0	1	1	Input 1
1	0	1	Input 2
1	1	1	Input 3

Original figure or table © 2001 by Addison Wesley Longman, Inc


Truth Table is now  
in Counting Order:

$E$	$S_1$	$S_0$	$Out$
0	X	X	Z
1	0	0	Input 0
1	0	1	Input 1
1	1	0	Input 2
1	1	1	Input 3

# Carpinelli Figure 1.9 (c), as it appears in the text:

Original figure or table © 2001 by Addison Wesley Longman, Inc
 
# Carpinelli Figure 1.9 (c), *CORRECTED*:



$S_1$	$S_0$	$E$	Output
X	X	1	Z
0	0	0	Input 0
0	1	0	Input 1
1	0	0	Input 2
1	1	0	Input 3

Original figure or table © 2001 by Addison Wesley Longman, Inc

Truth Table is now  
in Counting Order:

$E$	$S_1$	$S_0$	$Out$
0	0	0	Input 0
0	0	1	Input 1
0	1	0	Input 2
0	1	1	Input 3
1	X	X	Z


# Carpinelli Figure 1.10: CONSTRUCTION of a 4-1 MULTIPLEXOR from THREE 2-1 MULTIPLEXORS

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.11 (a), as it appears in the text: DECODER

Original figure or table © 2001 by Addison Wesley Longman, Inc
 
# Carpinelli Figure 1.11 (a), showing CORRECTION:




Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.11 (b), as it appears in the text:

Original figure or table © 2001 by Addison Wesley Longman, Inc
 
# Carpinelli Figure 1.11 (b), *CORRECTED*:



$S_1$	$S_0$	$E$	$O_0$	$O_1$	$O_2$	$O_3$
X	X	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

Original figure or table © 2001 by Addison Wesley Longman, Inc

Truth Table with several corrections, and in Counting Order:


$E$	$S_1$	$S_0$	$Out_0$	$Out_1$	$Out_2$	$Out_3$
0	X	X	Z	Z	Z	Z
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	1	1



# Carpinelli Figure 1.11 (c), as it appears in the text:

Original figure or table © 2001 by Addison Wesley Longman, Inc
 
# Carpinelli Figure 1.11 (c), *CORRECTED*:



$S_1$	$S_0$	$E$	$O_0$	$O_1$	$O_2$	$O_3$
X	X	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	0	1

Original figure or table © 2001 by Addison Wesley Longman, Inc

Truth Table with several corrections, and in Counting Order:

$E$	$S_1$	$S_0$	$Out_0$	$Out_1$	$Out_2$	$Out_3$
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	1	1
1	X	X	Z	Z	Z	Z


# Carpinelli Figure 1.12 (a): SIMPLE ENCODER

Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Figure 1.12 (b), as it appears in the text:**

**Original figure or table © 2001 by Addison Wesley Longman, Inc**
 
# Carpinelli Figure 1.12 (b), *CORRECTED*:



$I_0$	$I_1$	$I_2$	$I_3$	$E$	$S_1$	$S_2$	$V$
X	X	X	X	0	Z	Z	Z
0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1
0	1	0	0	1	0	1	1
0	0	1	0	1	1	0	1
0	0	0	1	1	1	1	1

Original figure or table © 2001 by Addison Wesley Longman, Inc


**Abbreviated Truth Table  
in Counting Order  
(not all input combinations are  
shown, since external constraints  
allow at most one input line  
to have a value of 1):**

$E$	$I_3$	$I_2$	$I_1$	$I_0$	$S_1$	$S_0$	$V$
0	X	X	X	X	Z	Z	Z
1	0	0	0	0	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	1	1
1	0	1	0	0	1	0	1
1	1	0	0	0	1	1	1


# Carpinelli Figure 1.12 (c), as it appears in the text:

Original figure or table © 2001 by Addison Wesley Longman, Inc
 
# Carpinelli Figure 1.12 (c), *CORRECTED*:



$I_0$	$I_1$	$I_2$	$I_3$	$E$	$S_1$	$S_2$	$V$
X	X	X	X	1	Z	Z	Z
0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	1
0	1	0	0	0	1	0	1
0	0	1	0	0	0	1	1
0	0	0	1	0	1	1	1

 

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Abbreviated Truth Table  
in Counting Order**  
(not all input combinations are shown, since external constraints allow at most one input line to have a value of 1):

$E$	$I_3$	$I_2$	$I_1$	$I_0$	$S_1$	$S_0$	$V$
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	1	0	0	0	1	1	1
1	X	X	X	X	Z	Z	Z

# Carpinelli Figure 1.13 (a): PRIORITY ENCODER

Original figure or table © 2001 by Addison Wesley Longman, Inc



# Carpinelli Figure 1.13 (b) and (c) PRIORITY ENCODER (alternative version)

Original figure or table © 2001 by Addison Wesley Longman, Inc


# Carpinelli Figure 1.14: ONE-BIT COMPARATOR

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.15, as it appears in the text: **SINGLE-BIT STAGE of a MULTI-BIT COMPARATOR**

Original figure or table © 2001 by Addison Wesley Longman, Inc
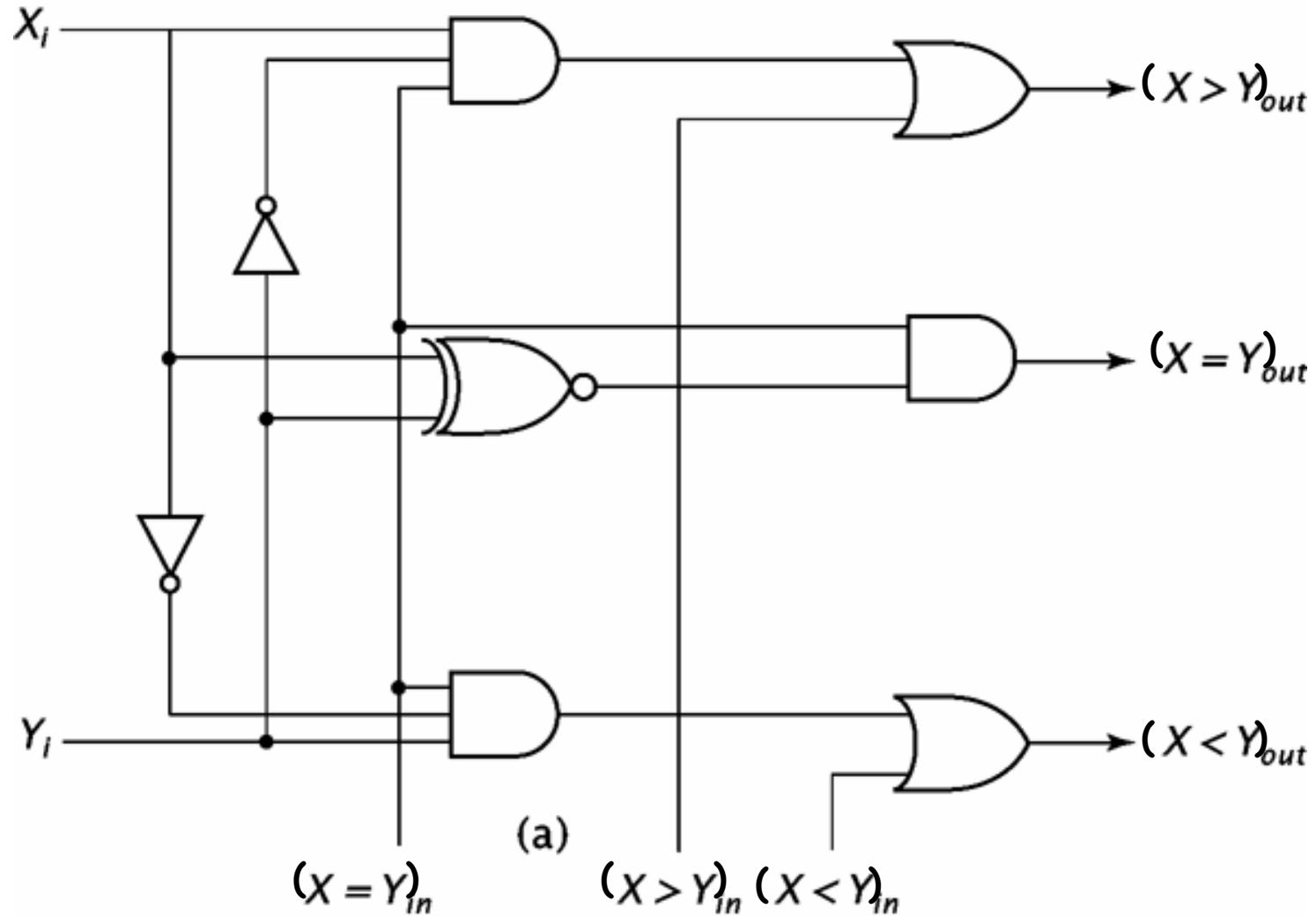
# Carpinelli Figure 1.15, *CORRECTED*: SINGLE-BIT STAGE of a MULTI-BIT COMPARATOR




Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.16, as it appears in the text:

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.16, *CORRECTED*:

 

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.17: HALF ADDER



Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Figure 1.18, as it appears in the text: FULL ADDER**

**Original figure or table © 2001 by Addison Wesley Longman, Inc**


  
# Carpinelli Figure 1.18, *CORRECTED*: FULL ADDER



X	Y	$C_{in}$	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




Original figure or table © 2001 by Addison Wesley Longman, Inc


# Carpinelli Figure 1.19, as it appears in the text: FOUR-BIT ADDER

Original figure or table © 2001 by Addison Wesley Longman, Inc
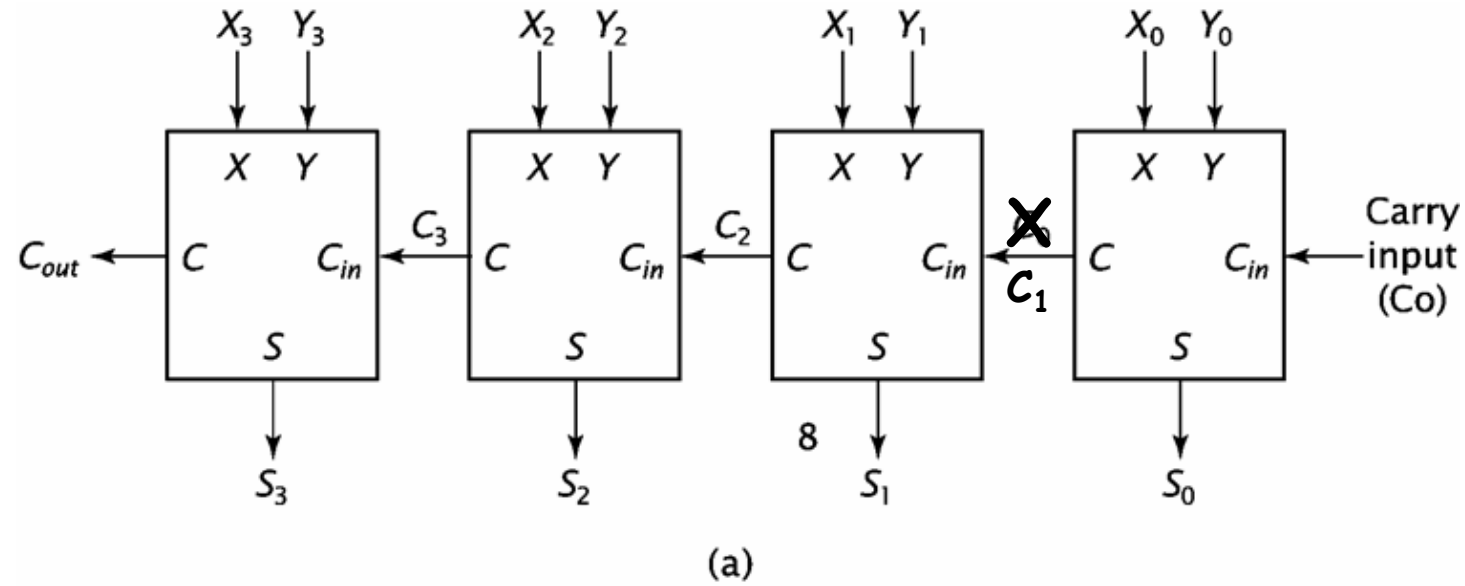
# Carpinelli Figure 1.19, CORRECTED: FOUR-BIT ADDER



 Original figure or table © 2001 by Addison Wesley Longman, Inc




# Carpinelli Figure 1.20: SUBTRACTOR

Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Figure 1.21, as it appears in the text: MEMORY MODULES**

Original figure or table © 2001 by Addison Wesley Longman, Inc
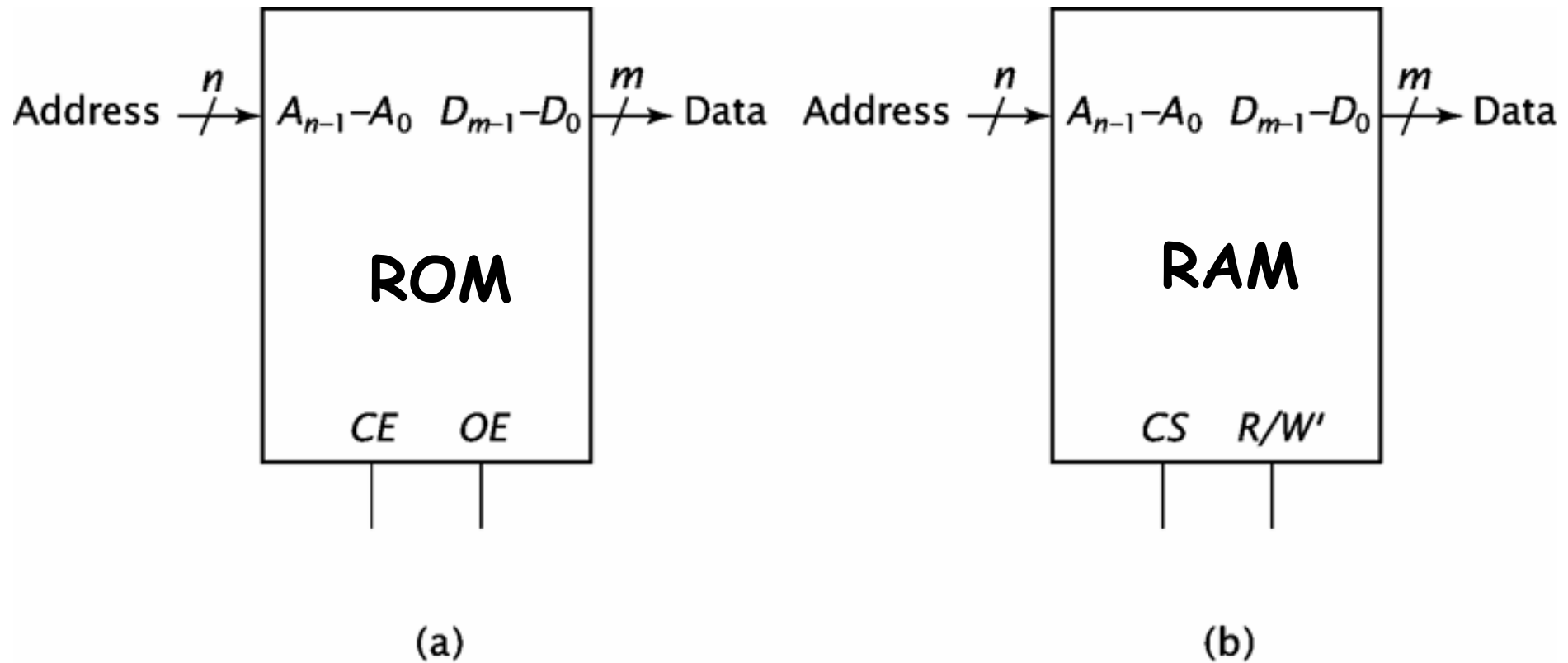
# Carpinelli Figure 1.21, *ENHANCED*: MEMORY MODULES



Original figure or table © 2001 by Addison Wesley Longman, Inc

# USE of MULTIPLE MEMORY MODULES

1. In general, a MEMORY consists of some number of addressable units, each of which is called a WORD.
2. The contents of a single word of memory are described as a string of bits. The words in a computer memory are all of identical width,  $w$ , and can be described as :

$$D_{(w-1)} \ D_{(w-2)} \ D_{(w-3)} \ . \ . \ . \ D_0.$$

3. For a memory containing a total of  $T$  words, it is necessary to specify a numeric address in order to be able to uniquely identify each word. For this purpose, some number of address bits is necessary. The required number of address bits is given by:

$$A \geq \lceil \log_2(T) \rceil$$

4. We can construct the memory from a number of memory modules of equal size. If each module contains  $N$  words, then the individual module requires  $n$  address bits to specify which word within the module is to be accessed. Since  $N$  is always an exact power of 2,

$$n = \log_2(N)$$

## USE of MULTIPLE MEMORY MODULES (continued)

5. For a total of  $T$  words, the number of modules (memory chips) required is:

$$M = T/N$$

$$\lceil \log_2 (M) \rceil = \lceil \log_2 (T) \rceil - \log_2 N$$

6. The total address lines are thus divided into two groups:  $m$  chip-select lines, and  $n$  within-chip word-select lines:

$$A = m + n$$


7. The  $n$  within-chip address lines are connected in parallel to the address-select input terminals of all of the memory modules.
8. The  $m$  chip-select lines go to an  $(m-x-2^m)$  decoder. Each output line from the decoder connects to the Chip-Enable input line of one memory chip.



# Carpinelli Figure 1.24 (a), as it appears in the text: TWO-NUMBER SORTER

Original figure or table © 2001 by Addison Wesley Longman, Inc
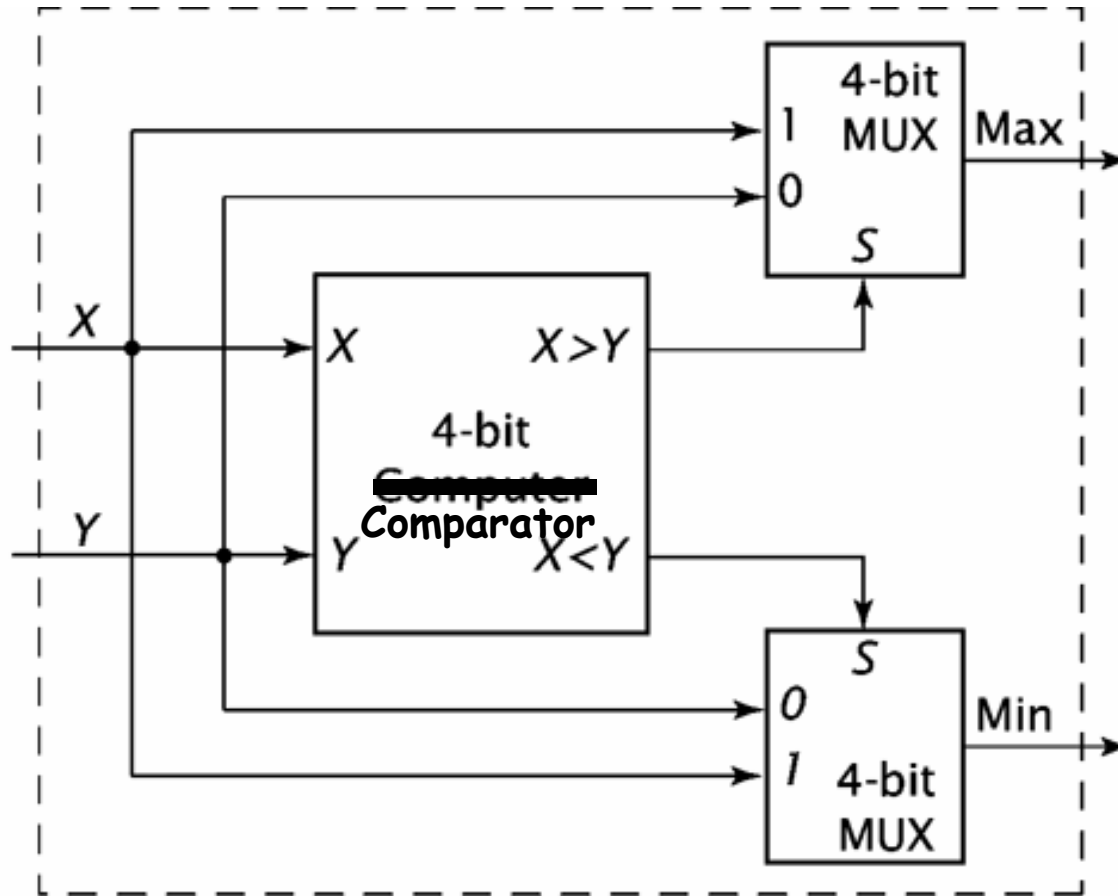
# Carpinelli Figure 1.24 (a), *CORRECTED*: TWO-NUMBER SORTER



Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Figure 1.24 (b): FOUR-NUMBER SORTER**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# TWO PRINCIPAL TYPES of LOGIC CIRCUITS:

1. COMBINATIONAL

2. SEQUENTIAL

# TWO PRINCIPAL TYPES of LOGIC CIRCUITS:

## 1. COMBINATIONAL

Current output (0s and 1s), after the passage of sufficient time to allow for circuit stabilization, is dependent solely upon current input (0s and 1s),

## 2. SEQUENTIAL

Current output depends not only on current input, but also on the prior history of the circuit state.

# Carpinelli Figure 1.25

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.26 (a): POSITIVE-EDGE-TRIGGERED D FLIP-FLOP

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.26 (b): POSITIVE-GATED D LATCH

Original figure or table © 2001 by Addison Wesley Longman, Inc



**Carpinelli Figure 1.27:  
POSITIVE-GATED D LATCH,  
with Asynchronous *SET* and *CLEAR***

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.28: SR LATCH

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 1.25:  
POSITIVE-EDGE-TRIGGERED JK FLIP-FLOP**

Original figure or table © 2001 by Addison Wesley Longman, Inc



**Carpinelli Figure 1.30:  
POSITIVE-EDGE-TRIGGERED T FLIP-FLOP**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.31, as it appears in the text: FOUR-BIT REGISTER (*not* a 4-Bit Flip-Flop)

Original figure or table © 2001 by Addison Wesley Longman, Inc
 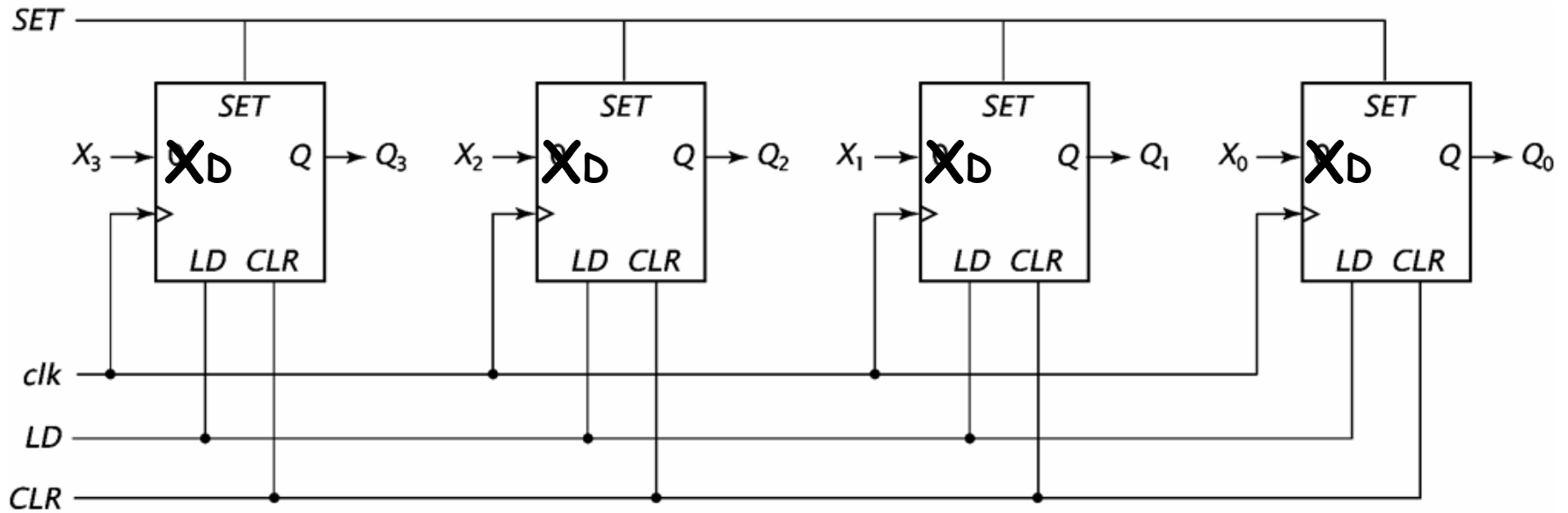
# Carpinelli Figure 1.31, *CORRECTED*: FOUR-BIT REGISTER (not a 4-Bit Flip-Flop)




Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.32, as it appears in the text: Four-Bit Incrementing (“Up”) Counter

Original figure or table © 2001 by Addison Wesley Longman, Inc
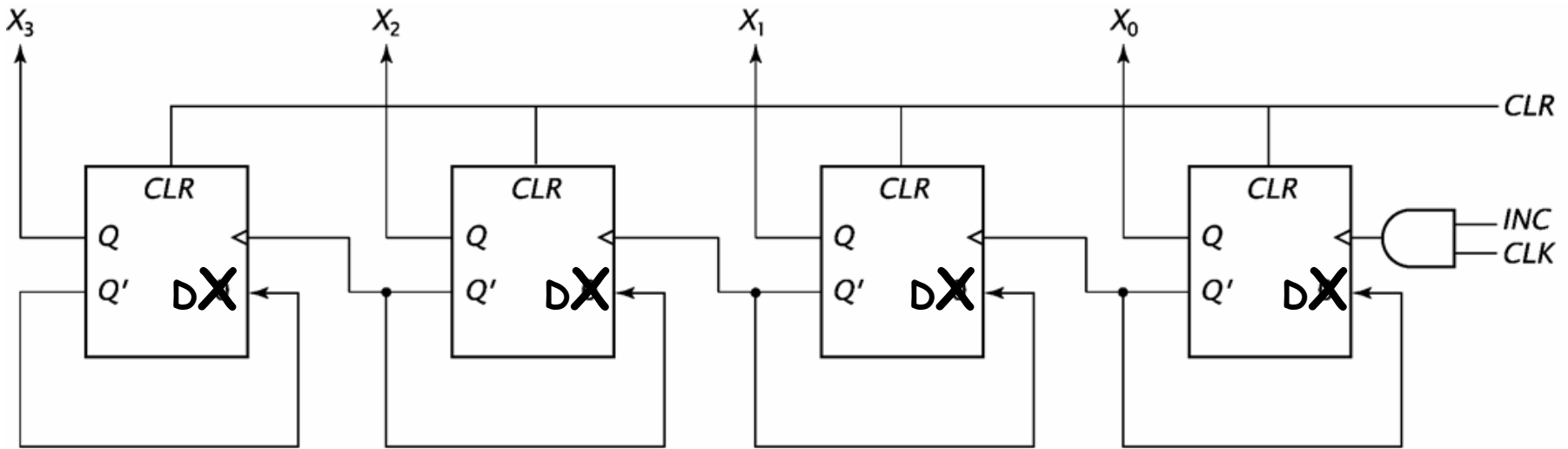
# Carpinelli Figure 1.32, *CORRECTED*: Four-Bit Incrementing (“Up”) Counter



CLR	INC	CLK	$X_{3-0}$
1	X	X	0
0	0	X	$X_{3-0}$
0	1	not $\uparrow$	$X_{3-0}$
0	1	$\uparrow$	$X_{3-0} + 1$

Original figure or table © 2001 by Addison Wesley Longman, Inc



# Carpinelli Figure 1.33: FOUR-BIT INCREMENTING/DECREMENTING COUNTER (“Up/Down” Counter)

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.34: FOUR-BIT LEFT-SHIFT REGISTER

Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Table 1.8, as it appears in the text: SHIFT OPERATIONS**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Table 1.8, *CORRECTED*: SHIFT OPERATIONS

The corrected version corresponds to the definitions of the various types of shift operations typically implemented in the Arithmetic Logic Unit (ALU) portion of Central Processing Units (CPUs).

Shift type	Mnemonic	$X$
Logical <del>linear</del> shift left	shl	<del><math>X_2 X_1 X_0 X_1</math></del> $X_2 X_1 X_0 0$
Logical <del>linear</del> shift right	shr	<del><math>X_2 X_1 X_0 X_1</math></del> $0 X_3 X_2 X_1$
Circular shift left	cil	$X_2 X_1 X_0 X_3$
Circular shift right	cir	$X_0 X_3 X_2 X_1$
Arithmetic shift left	ashl	<del><math>X_3 X_2 X_1 X_0</math></del> $X_2 X_1 X_0 0$
Arithmetic shift right	ashr	$X_3 X_3 X_2 X_1$

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.35: PROGRAMMABLE LOGIC ARRAY (PLA)

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 1.36: PROGRAMMABLE ARRAY of LOGIC (PAL)

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Problem 1.9:

$$\begin{aligned} F &= WXY' + WXZ + W'XY + XYZ' \\ &= (WXY'Z + WXY'Z') + (WXYZ + WXY'Z) + (W'XYZ + W'XYZ') + (WXYZ' + W'XYZ') \end{aligned}$$

Original figure or table © 2001 by Addison Wesley Longman, Inc

# CARRY-LOOKAHEAD ADDER

$$g_i = X_i \wedge Y_i$$

$$p_i = X_i + Y_i \text{ (not } X_i \oplus Y_i)$$



**FINITE-STATE MACHINES:  
SEQUENTIAL and COMBINATIONAL LOGIC**

# Carpinelli Figure 2.1 (a): GENERIC STATE-MACHINE MODEL

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 2.3: STATE DIAGRAMS for the JK FLIP-FLOP

Original figure or table © 2001 by Addison Wesley Longman, Inc

# Carpinelli Figure 2.4: *JK* FLIP-FLOP

State Table:

State Diagram:

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 2.5 (b):  
STATE DIAGRAM for the MODULO-6 COUNTER:  
MOORE MACHINE**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 2.6 (b):  
STATE DIAGRAM for the STRING-CHECKER:  
MOORE MACHINE**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 2.A (b):  
STATE DIAGRAM for the STRING-CHECKER  
with REVISED STATE ASSIGNMENTS:  
MOORE MACHINE**


Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 2.7,  
as it appears in the text:  
STATE DIAGRAM for the  
TOLL-BOOTH  
CONTROLLER:  
MOORE MACHINE**

Original figure or table © 2001 by Addison Wesley Longman, Inc



 **Carpinelli Figure 2.7,  
CORRECTED:  
STATE DIAGRAM for the  
TOLL-BOOTH  
CONTROLLER:  
MOORE MACHINE**



Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Table 2.5:  
STATES for the TOLL-BOOTH CONTROLLER:  
MOORE MACHINE**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Table 2.6:  
STATE TABLE for the TOOL-BOOTH CONTROLLER:  
MOORE MACHINE**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 2.8 (b):  
STATE DIAGRAM for the MODULO-6 COUNTER:  
MOORE MACHINE (Assigned State Values Included**

Original figure or table © 2001 by Addison Wesley Longman, Inc

# **Carpinelli Figure 2.10 (a): GENERIC MOORE MACHINE**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 2.10 (b):  
MOORE MACHINE IMPLEMENTATION of the  
MODULO-6 COUNTER**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**Carpinelli Figure 2.11:  
KARNAUGH MAPS for the NEXT STATE  
of the MODULO-6 COUNTER**

Original figure or table © 2001 by Addison Wesley Longman, Inc

**END**